



# Architecture Design

Alexander Standaert  
Wouter Diels

# OUTLINE

- **ARCHITECTURE AND TIMING**
- **DECODERS**
- **SENSE AMPLIFIERS**
- **LOAD**
- **PLANNING AND CONTENT TABLE**
- **CONCLUSION** : Conclusion and Future work


# TIMING (I)

 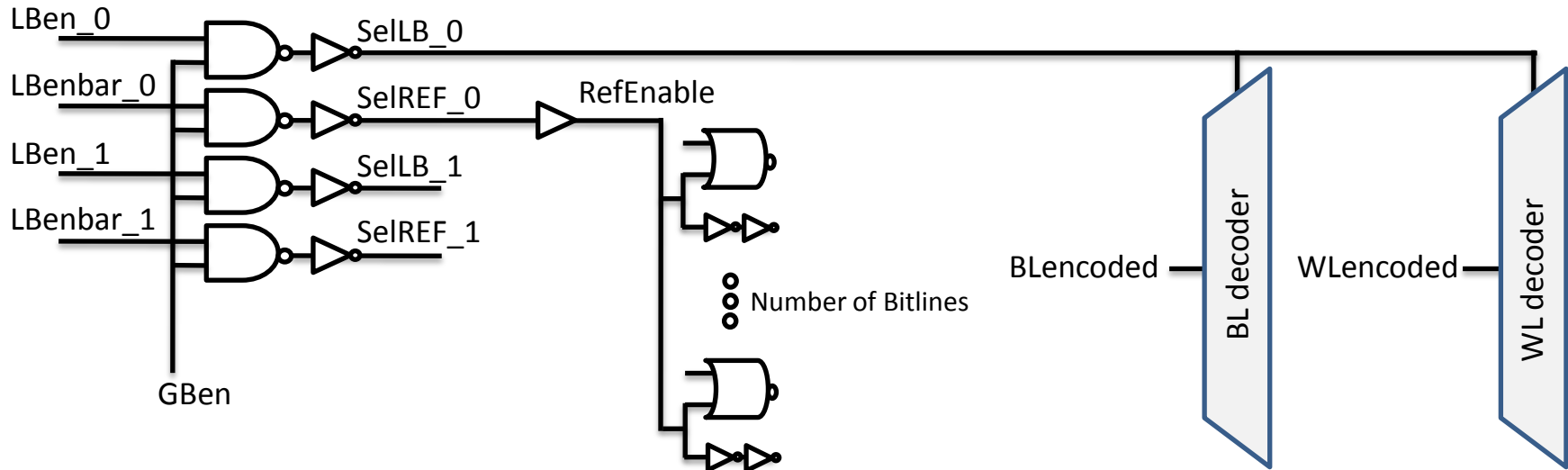


## Constraints / Optimization

1.  $T_1 \approx T_2$  : cell should be selected when the load is turned on, if not  $\rightarrow$  dead time. (BL and WL decoder same size)
2.  $T_1 \approx T_3$  : if  $T_1 > T_3$  ref is selected before mem  $\rightarrow$  energy waste (Design non optimal ref buffer)


# REFERENCE ARRAY: Buffers

 



 
Buffer designed with logical effort  
(stage effort = 4)



RefEnable

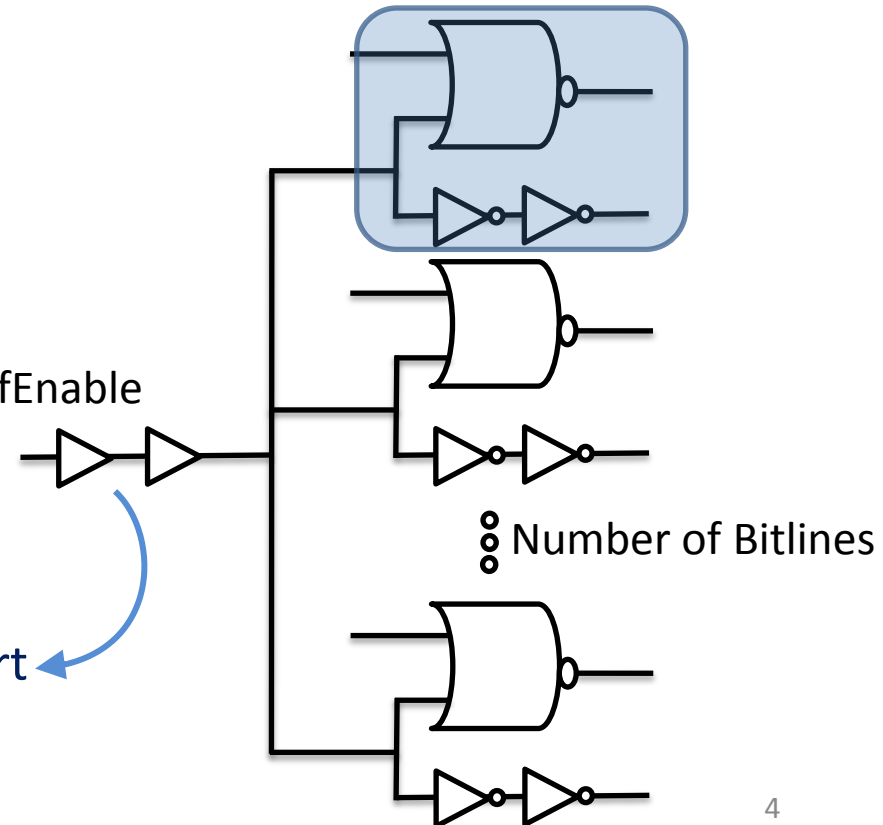




# TIMING (2)

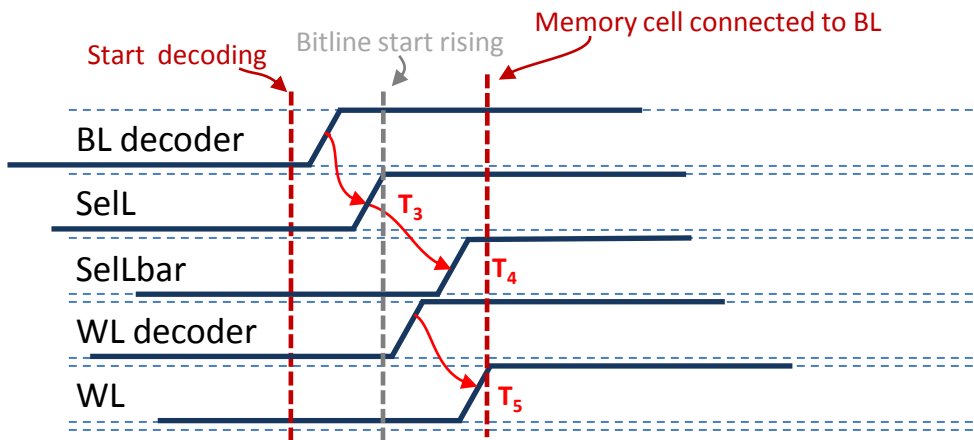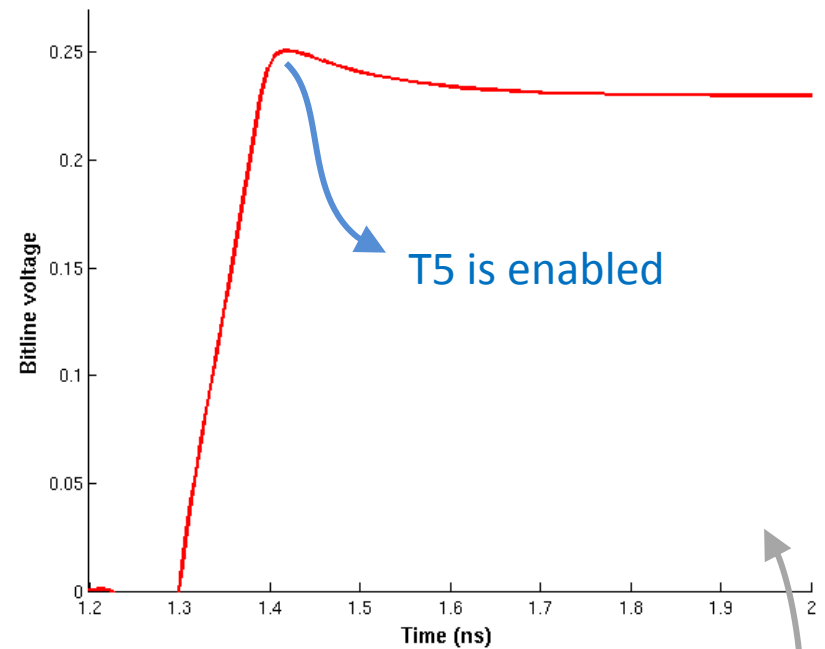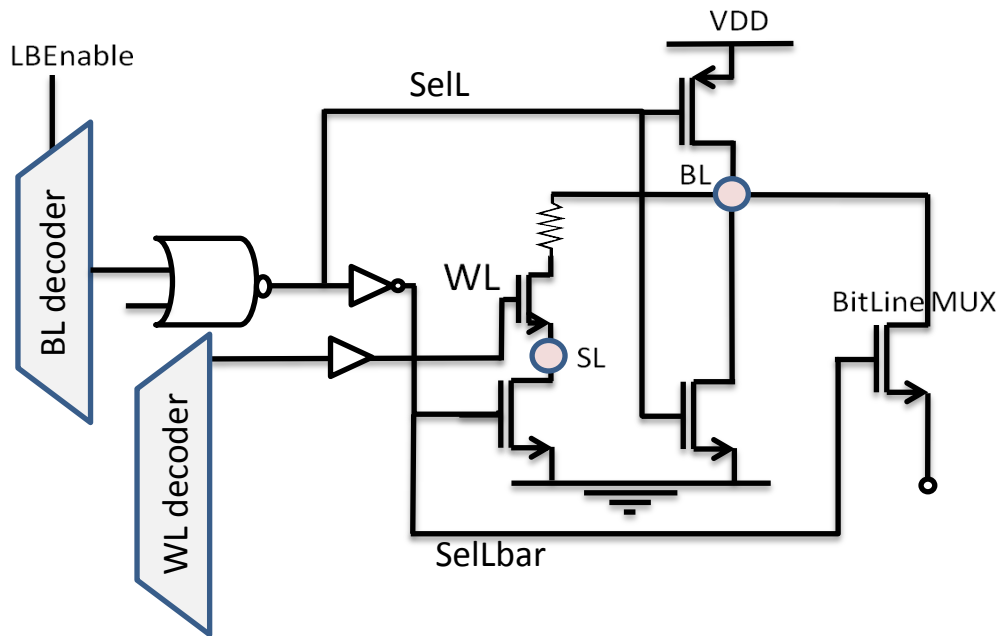

## Constraints / Optimization

- cell should be selected when load is turned on  $\rightarrow T_3 \approx T_4 \approx T_5$ .  $T_3 < T_4$  because of inverter.  $T_5$  is dependent of size of BL and WL decoders. When  $T_3 < T_4, T_5$  the bitline is rising without cell selected

## TIMING (3)

  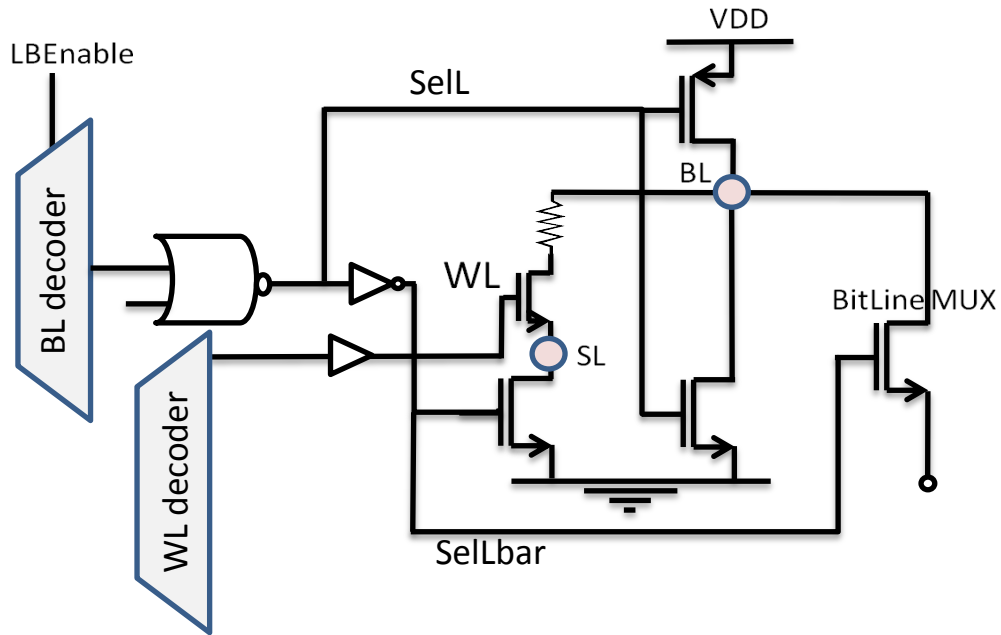



## Constraints / Optimization

4. cell should be deselected when load is turned off  $\rightarrow T_3 \approx T_4 \approx T_5$ .  $T_3 < T_4$  because of inverter.  $T_5$  is dependent of size of BL and WL decoders. When  $T_3 > T_5$  the bitline is rising without cell selected

$6 \times 10^{-10}$ 

- 

## TIMING (5)

 
 


## Constraints / Optimization

5. ref should be selected when load is turned on  $\rightarrow T_6 \approx T_7 \approx T_8$ .  
 $T_6 < T_7$  because of inverter.  $T_8$  is dependent of delay element (2 inverters)



# TIMING (6)

  

## Constraints / Optimization

6. ref should be selected when load is turned off  $\rightarrow T_9 \approx T_{10} \approx T_{11}$ .  
 $T_9 < T_{10}$  because of inverter.  $T_{11}$  is dependent of 2 inverters

# TIMING (7)

	Affects	Implies
(1)	Speed	$\#WL \approx \#BL$
(2)	Energy	/
(3)	Speed	$\#WL < \#BL$
(4)	Clean signals	$\#WL > \#BL$
(5)	Speed	$T_{\text{delay}} < T_{\text{nor} + \text{inv}}$
(6)	Clean signals	$T_{\text{delay}} > T_{\text{nor} + \text{inv}}$

Could try to extend ref delay to compensate energy wast in bitlines but time is too short  
→ Don't connect all the ref cells to bitline

# ADDRESSING


Use not fully coded address (number of bits = 24??)

address_GB	select_LB0	select_LB1	address_BL	address_WL
------------	------------	------------	------------	------------

Consider address bit voltage to come from ideal voltage source

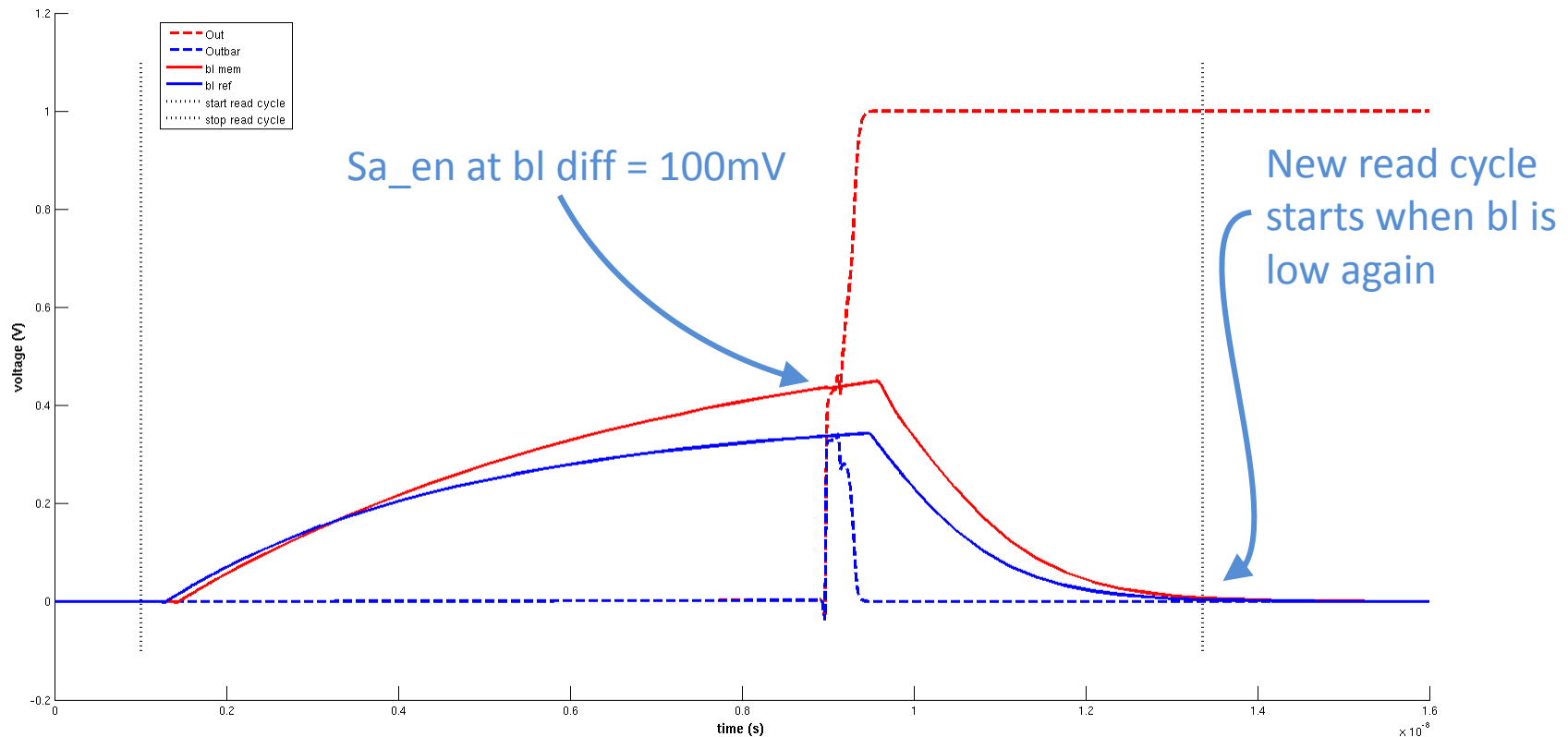
# ARCHITECTURE (I)

- Find all possible solutions for #WL, #BL, #GB in the range  $2^{3-9}$
  - That comply to the following constraints:
    - # cells = 4194304 (4MB)
    - # BL  $\leq$  #WL
  - Simulate as follows:
- 20 solutions




- Add initial conditions to nodes to get a quicker convergence in dc op point

# ARCHITECTURE (2)

 

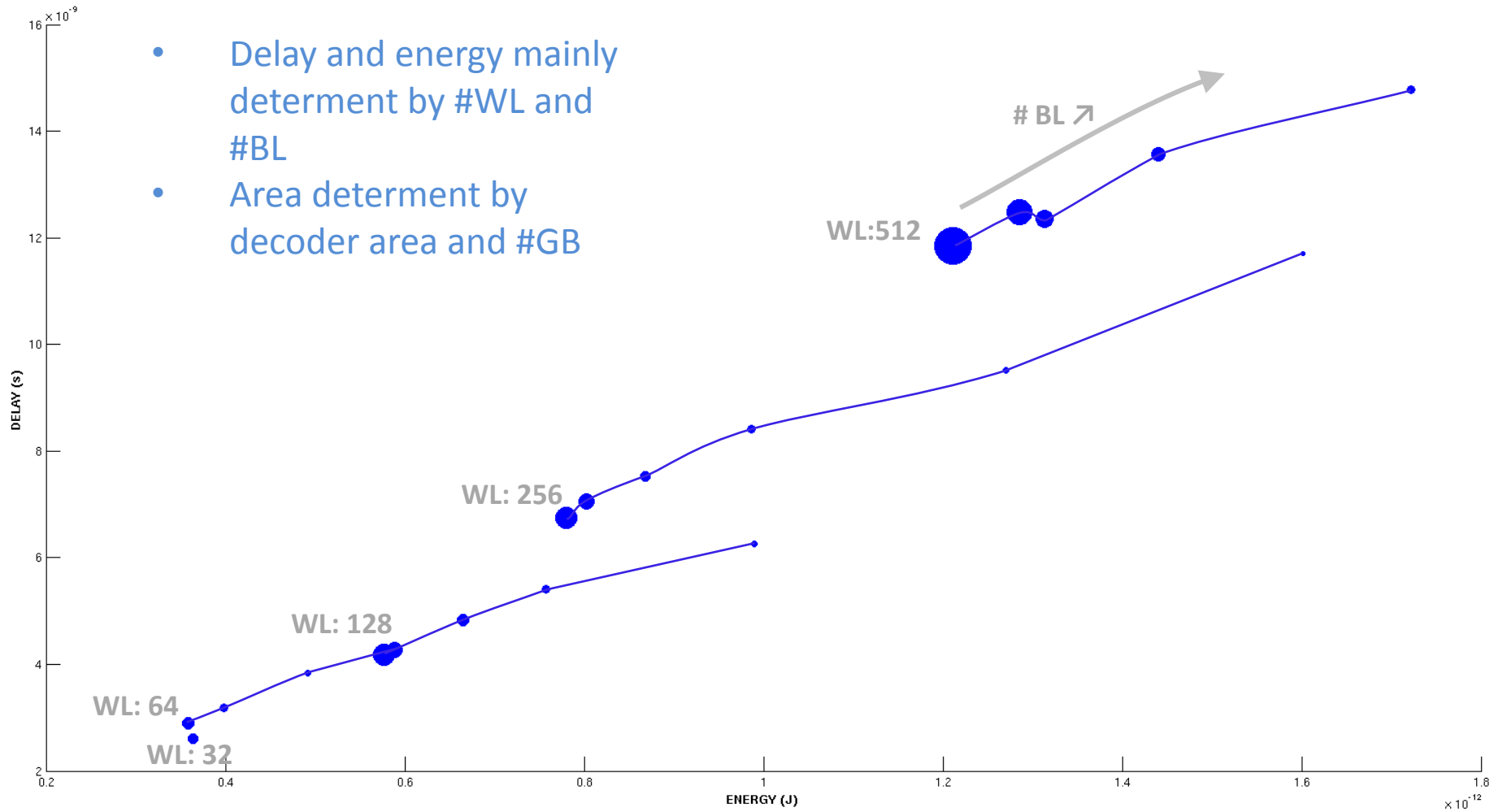
# ARCHITECTURE (2)

- Delay and energy mainly determent by #WL and #BL
- Area determent by decoder area and #GB



# ARCHITECTURE (3)

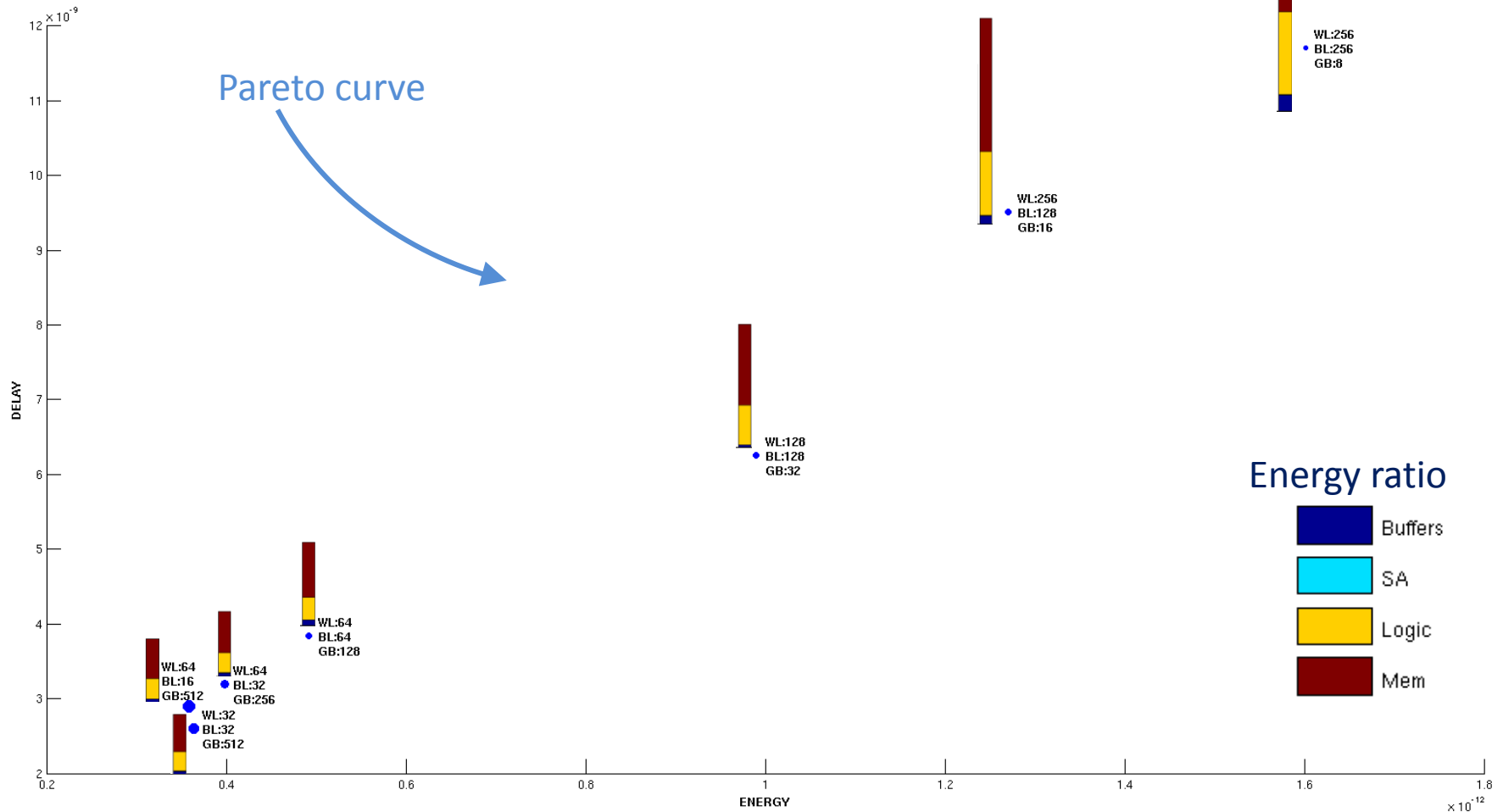

Leakage energy is 2 orders of magnitude smaller

# OUTLINE

- **ARCHITECTURE AND TIMING**

- **DECODERS**

- **SENSE AMPLIFIERS**


- **LOAD**

- **PLANNING AND CONTENT TABLE**

- **CONCLUSION** : Conclusion and Future work


# DECODERS (I)

## Type 1

 

- Delay dependent of previous and current address
- Prone to glitches


## Type 2

 


- Delay more or less constant for each address
- Delay and Energy are more robust against mismatch



## DECODERS (2)


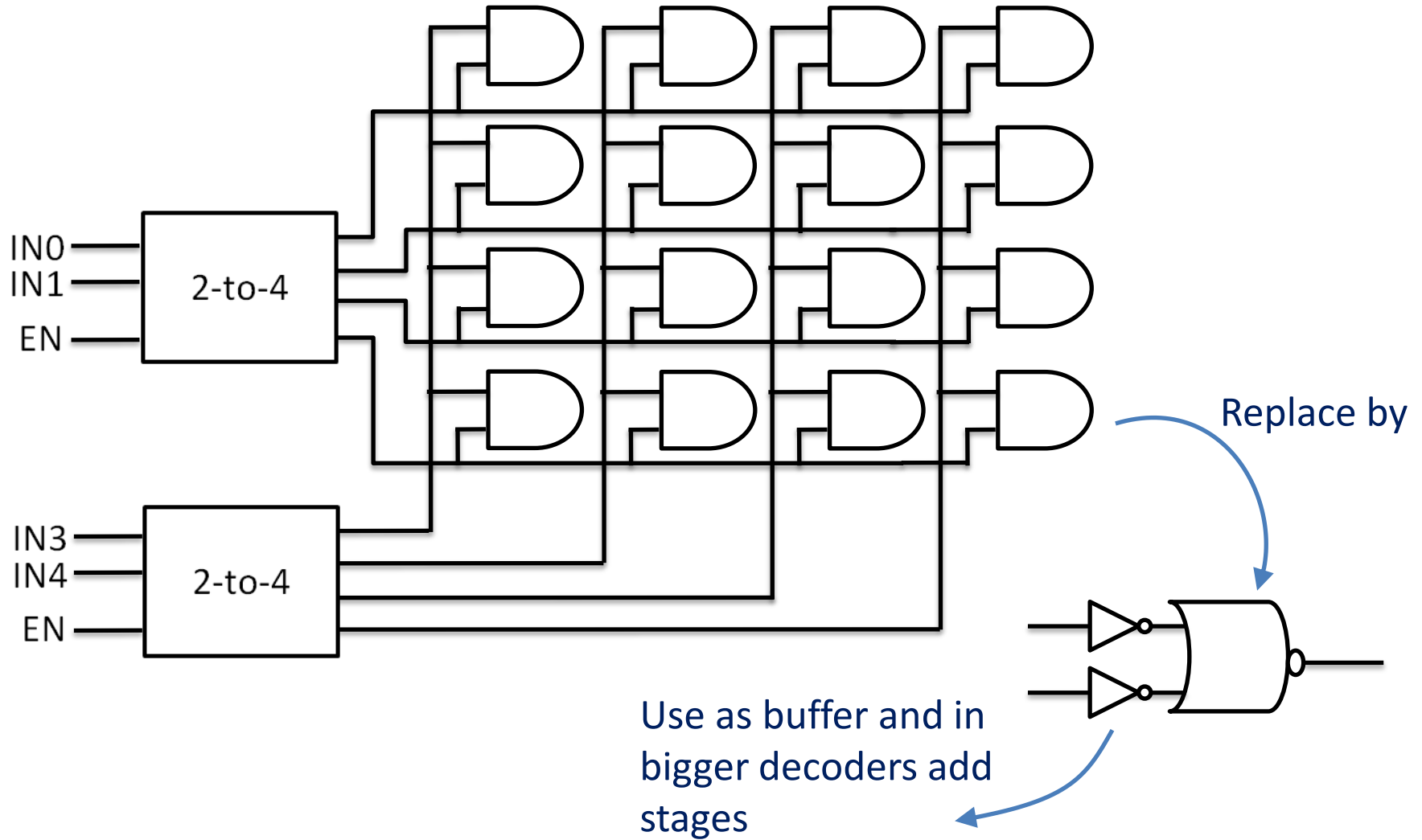


# DECODERS (3)

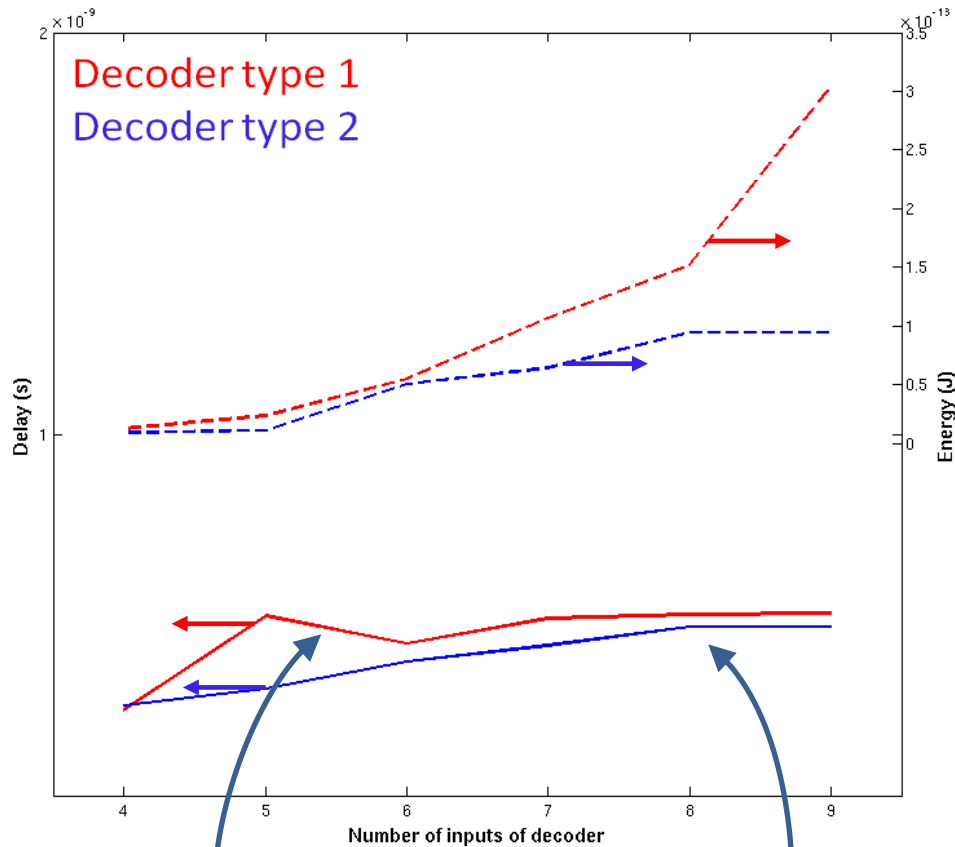

← Worst case delay and energy at worst case delay ( $\neq$  worst case energy !!!)

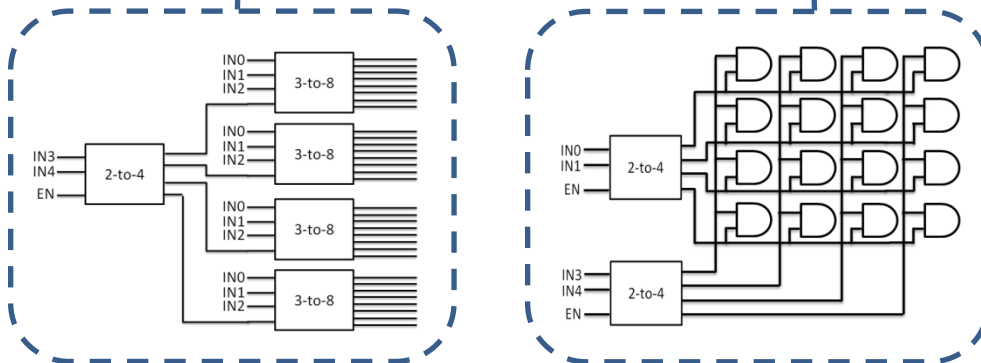 ↓ Total area ( $F^2$  = min technology area)



# OUTLINE


- **ARCHITECTURE AND TIMING**
- **DECODERS**
- **SENSE AMPLIFIERS**
- **LOAD**
- **PLANNING AND CONTENT TABLE**
- **CONCLUSION** : Conclusion and Future work

# Sense Amplifier



- Sensitivity analysis
- Sweep  $V_t$ - &  $\beta$ -mismatch of different transistors independently and manually
- Offset as function of variation instances
- Done for minimal SA, since no idea yet of sizes to be used in our architecture

# Sensitivity results

**V<sub>t</sub>-variations**

 


**β-variations**

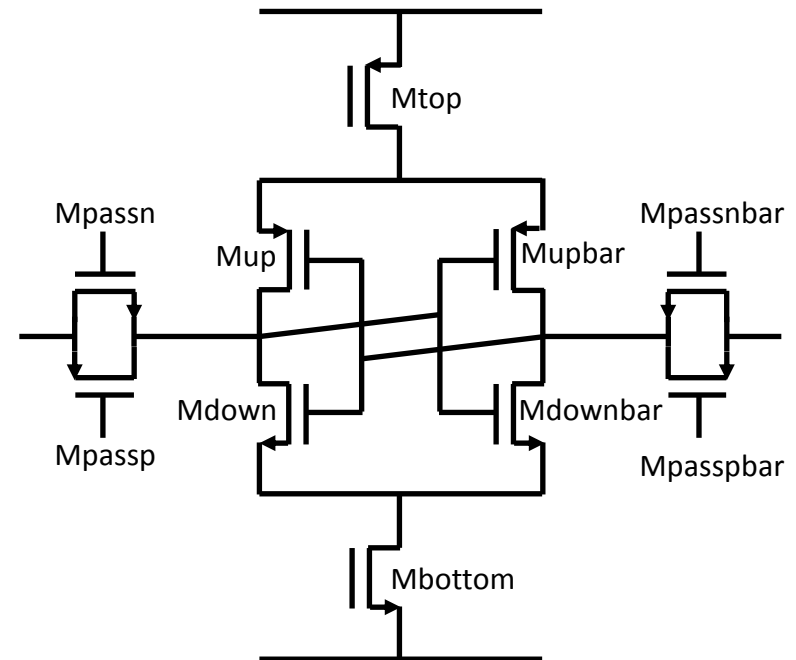 

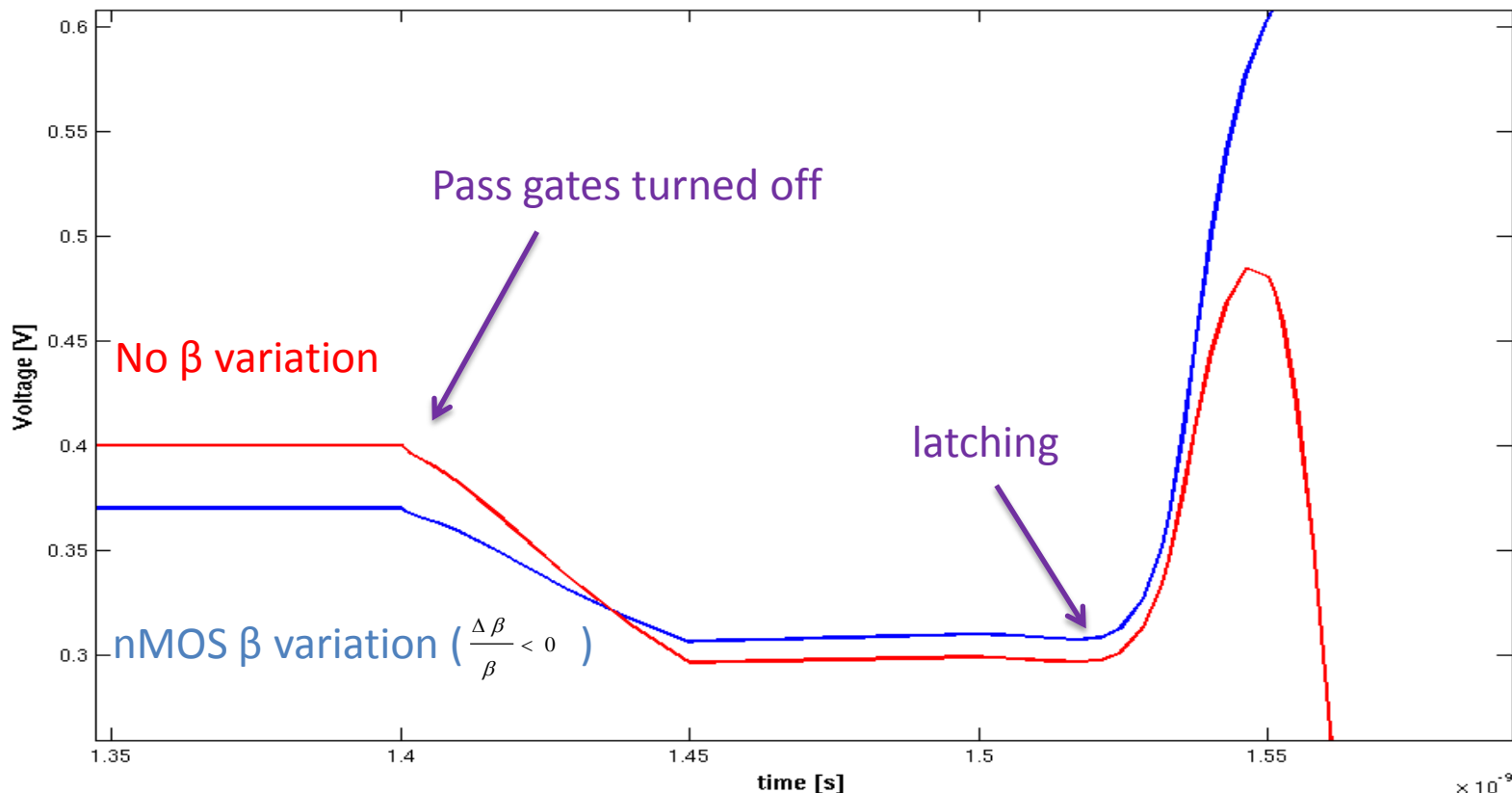
# Sensitivity Analysis

- Mainly contributions by differential pair
- Also  $\beta$ -variations pass-gates:  
charge injection not matched anymore



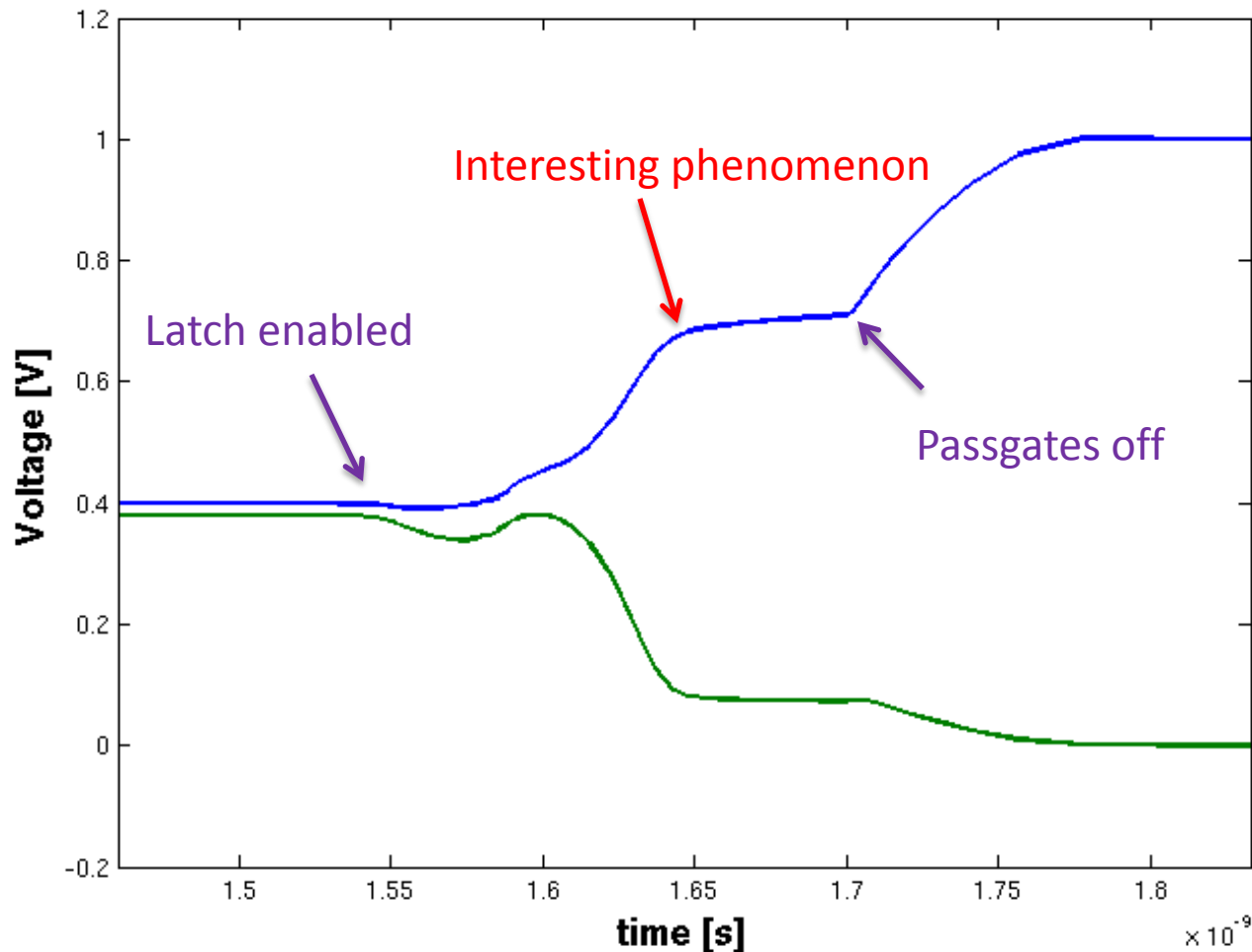
# Pass Gate mismatch

- Avoid by allowing (short) overlap PassEnable & LatchEnable



# Diels effect ©®


(minimal SA)

 




 
# Diels effect ©®

- Depending on resistance value, strange dynamic behaviour.


  
# Diels effect ©®

- Capacitor acts as short in beginning
- Ordinary voltage drop over resistor, output charges normally (high frequencies)
- Afterwards also charging C



## Diels effect ©®

- Out(bar) charges almost linearly
- AC voltage over capacitor almost zero
- Latching and RC-charging are separated
- Vc response for linearly charging source

$$v_c(t) = t - RC \left(1 - e^{-\frac{t}{RC}}\right)$$


- RC-product must be large enough in order for C-short approximation to hold

## Diels effect ©®

- When RC-product is too small:
- Latching and RC-charging no longer separated
- Difficult to mathematically describe
 
# Sense amplifier pareto


- Very large simulation
- Pareto surface delay-energy- $\Delta V$



# OUTLINE

- **ARCHITECTURE AND TIMING**
- **TIMING**
- **SENSE AMPLIFIERS**
- **LOAD**
- **PLANNING AND CONTENT TABLE**
- **CONCLUSION** : Conclusion and Future work

# LOAD


 


Size x 4 for mismatch

$$\rightarrow 3\sigma_{\text{Vdiff}} = 29\text{mV}$$

$$\rightarrow V_{\text{cell max}} = 176\text{mV (after mc)}$$

(todo schrijf hoe berekend)

  

# OUTLINE

- **ARCHITECTURE AND TIMING**
- **TIMING**
- **SENSE AMPLIFIERS**
- **LOAD**
- **PLANNING AND CONTENT TABLE**
- **CONCLUSION** : Conclusion and Future work



# OUTLINE

- **ARCHITECTURE AND TIMING**
- **TIMING**
- **SENSE AMPLIFIERS**
- **LOAD**
- **PLANNING AND CONTENT TABLE**
- **CONCLUSION** : Conclusion and Future work