


Architecture Design

Alexander Standaert
Wouter Diels


OUTLINE

- **REFERENCE ARRAY**
- **DECODERS + BUFFERS**
- **VDD/SPEED TEST**
- **CONDOR**
- **ARCHITECTURE ANALYSIS**
- **CONCLUSION** : Conclusion and Future work


REFERENCE ARRAY

 


REFERENCE ARRAY

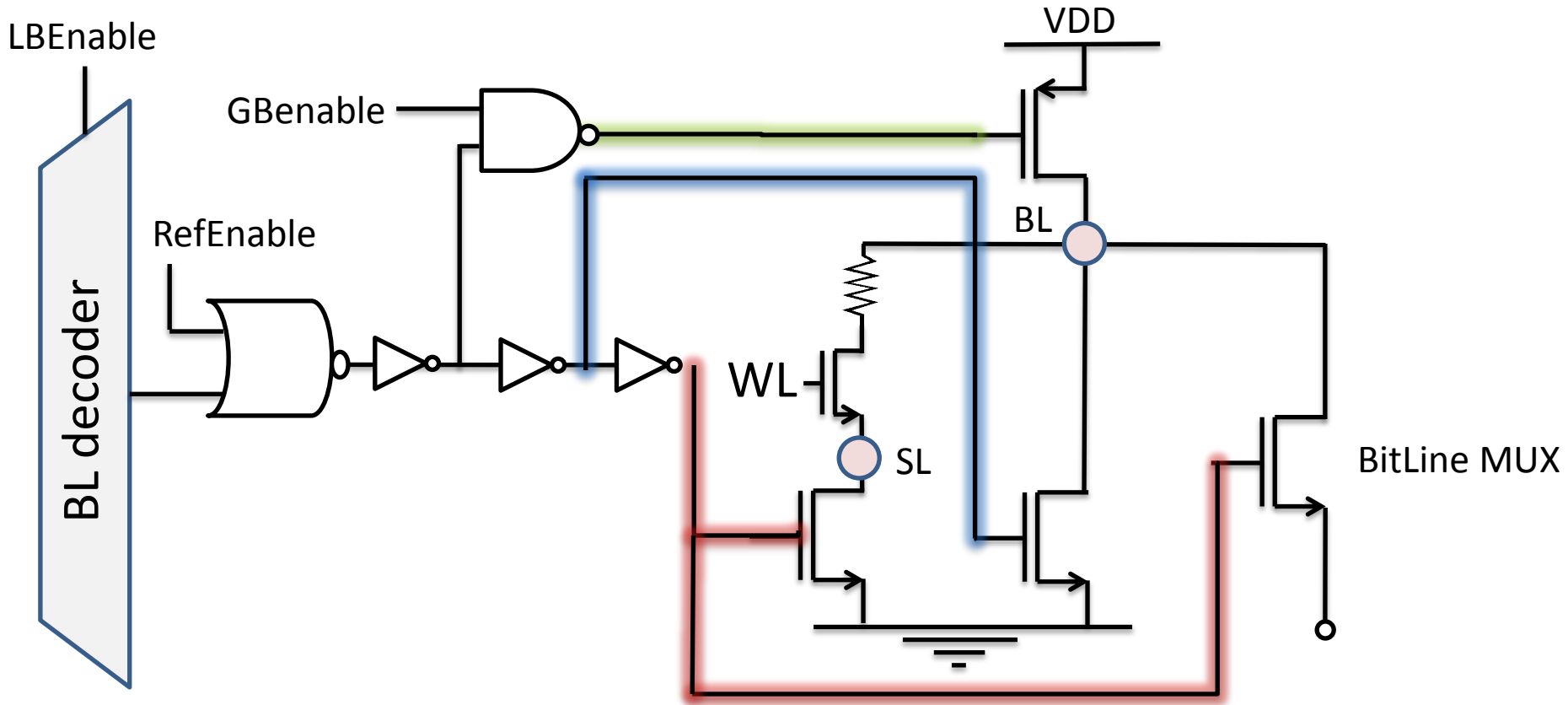


REFERENCE ARRAY

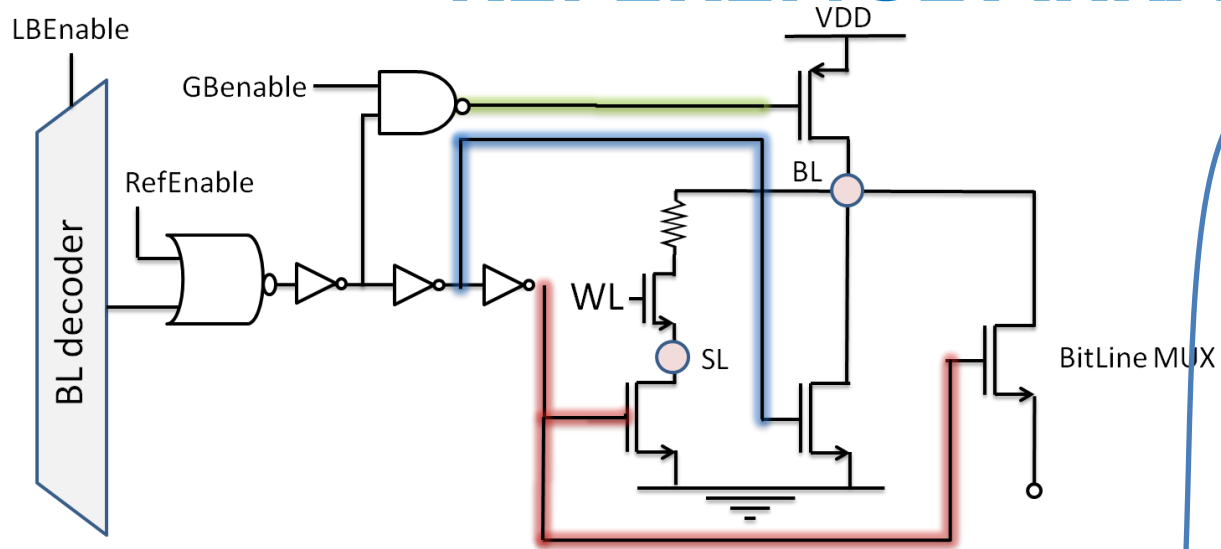

 
WL_ref = RefEnable
→ Load is still on when
all the rest is of



REFERENCE ARRAY

 

 BitLine Mux is turned off before the node is fully discharged. Charge trapped is really small and doesn't affect next read cycle





OUTLINE

- **REFERENCE ARRAY**
- **DECODERS + BUFFERS**
- **VDD/SPEED TEST**
- **CONDOR**
- **ARCHITECTURE ANALYSIS**
- **CONCLUSION** : Conclusion and Future work



Decoders

  - Netlist allows sizing every CMOS gate.
- Based on cascading 2-to-4 decoders and 3-to-8 decoders




Decoders

  - Glitches because NOR-gated output
- Solve by using NAND + Inverter Decoder topology, more area, worth it?




BL Decoders

 - BL capacitance increases when more cells per BL
- Delay increases too
- Can't decrease Pull-Up resistance because BL will be charged to VDD
- Limited #WLpB
- No sizing needed for BL decoders



WL Decoders: optimization

 
- Sizing every CMOS block difficult:
 - Different paths towards output consisting of different amount of stages and logical efforts
- Solution: Minimal decoder with sized inverter chain at output towards WL?



OUTLINE

- **REFERENCE ARRAY**
- **DECODERS + BUFFERS**
- **VDD/SPEED TEST**
- **CONDOR**
- **ARCHITECTURE ANALYSIS**
- **CONCLUSION** : Conclusion and Future work

VDD/SPEED TEST

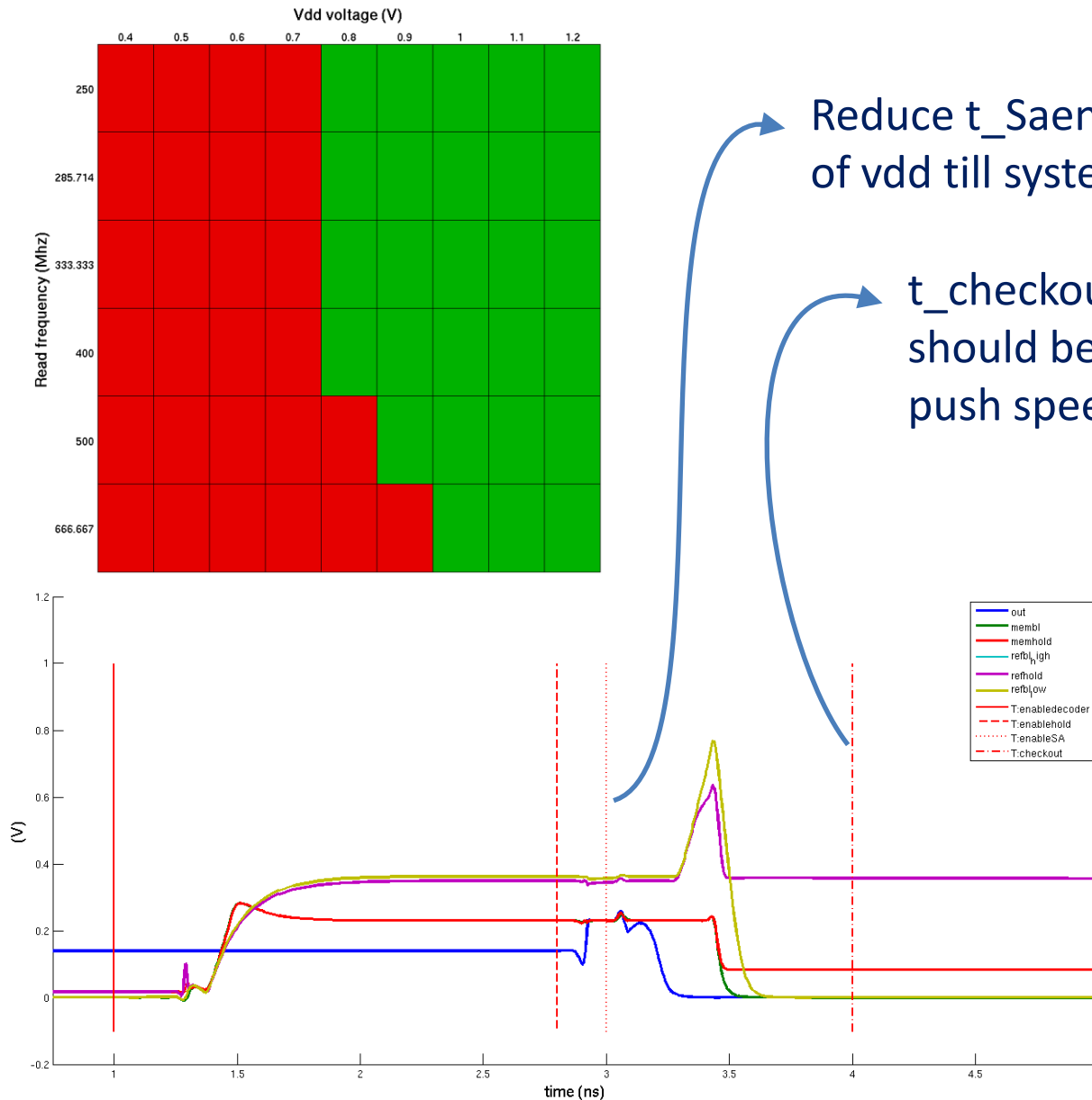

Reduce t_{Saenable} for different values of vdd till system fails.

t_{checkout} is cnt for now, but we should be able to decrease it to push speed limit futher

NOTE : no mismatch yet because SA is not yet sized !!!

OUTLINE

- **REFERENCE ARRAY**
- **DECODERS + BUFFERS**
- **VDD/SPEED TEST**
- **CONDOR**
- **ARCHITECTURE ANALYSIS**
- **CONCLUSION** : Conclusion and Future work

CONDOR



- Grid computing system
- Introduced at VISICS by Bert Deknuydt
- Last week we got it working with Mat2Spice and Spectre
- Documentation and new version Mat2Spice can be found on the wiki

<https://wiki.esat.kuleuven.be/visics/condor>

- It is currently looked into getting it installed in the pc rooms

OUTLINE

- **REFERENCE ARRAY**
- **DECODERS + BUFFERS**
- **VDD/SPEED TEST**
- **CONDOR**
- **ARCHITECTURE ANALYSIS**
- **CONCLUSION** : Conclusion and Future work

OUTLINE


- **REFERENCE ARRAY**
- **DECODERS + BUFFERS**
- **VDD/SPEED TEST**
- **CONDOR**
- **ARCHITECTURE ANALYSIS**
- **CONCLUSION** : Conclusion and Future work

Future work

- Determine worst case decoder delay (MonteCarlo)
- Research optimal architecture parameters
Probably need to trim netlist to achieve acceptable simulation time
- Inverter chain to buffer RefEnable (huge load to drive)
- Optimize decoders? (and calculate decoder area)
- Automate timing signals for Sense Amplifier

Main architecture


CELL

 


In this topology one sourceline
and charge/discharge per bitline
Ideal?

BRANCH

#WLpB Data cells
1 Ref cell

 

Main architecture (cont.)

 


Local Block

#BLpLB Branches

→ #BLpLB * #WLpB Data cells

→ #BLpLB Ref cells

 Global Block **Main architecture (cont.)**





Architecture parameters

- # Global Blocks
- # BitLines per Local Block
- # WordLines per Branch

Total number of cells = $2 * \text{NoGB} * \text{NoBLpLB} * \text{NoWLpB}$



Decoders

  - Netlist allows sizing every CMOS gate.
- Based on cascading 2-to-4 decoders and 3-to-8 decoders




Decoders

 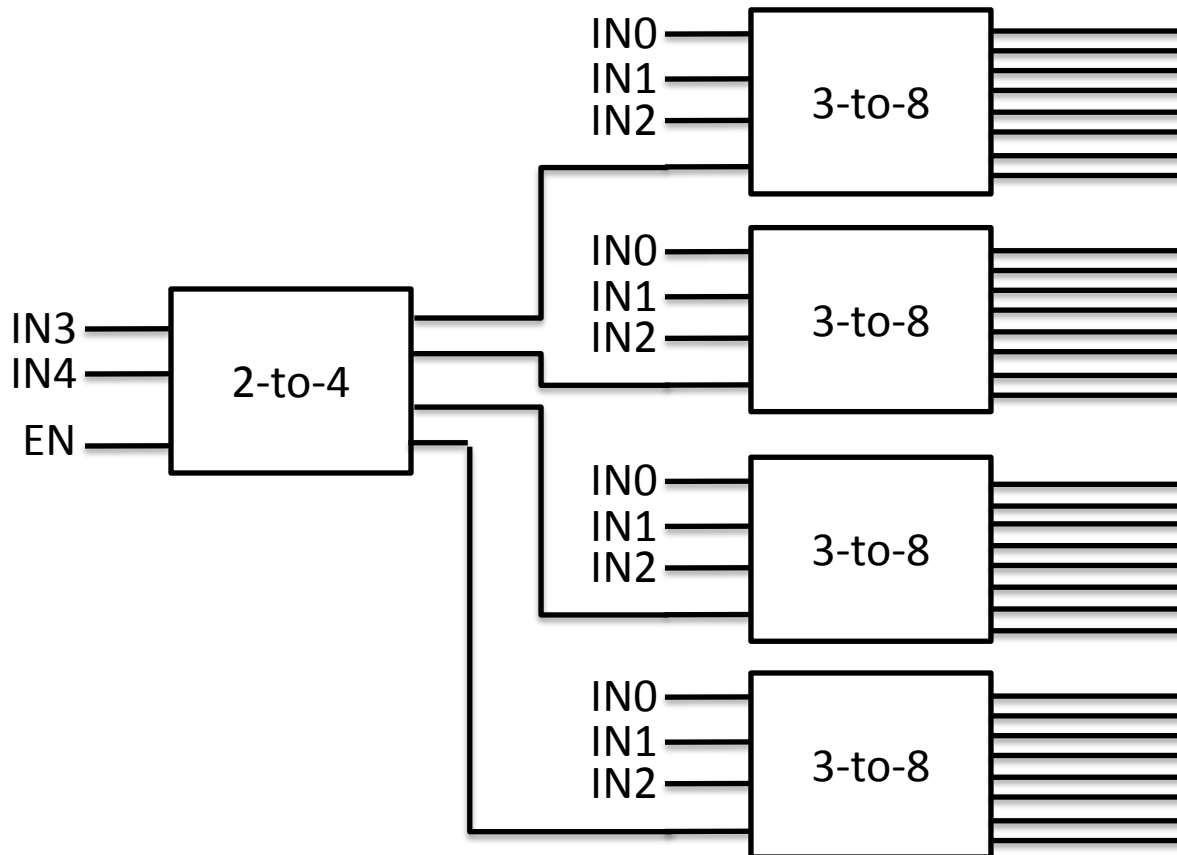- Glitches because NOR-gated output
- Solve by using NAND + Inverter Decoder topology, more area, worth it?




BL Decoders

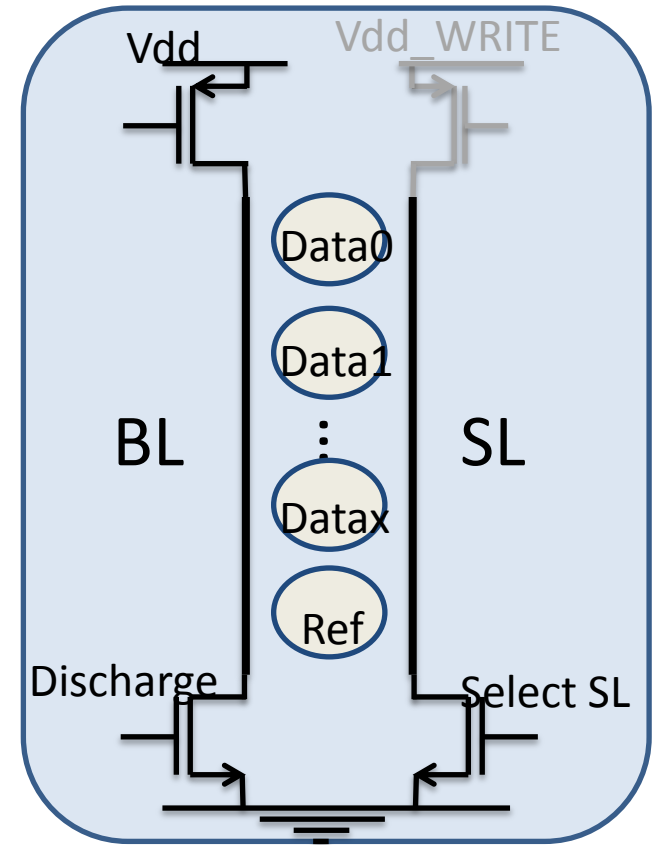- BL capacitance increases when more cells per BL
- Delay increases too
- Can't decrease Pull-Up resistance because BL will be charged to VDD
- Limited #WLpB
- No sizing needed for BL decoders




WL Decoders: optimization

 - Sizing every CMOS block difficult:
 - Different paths towards output consisting of different amount of stages and logical efforts
- Solution: Minimal decoder with sized inverter chain at output towards WL?




Timing

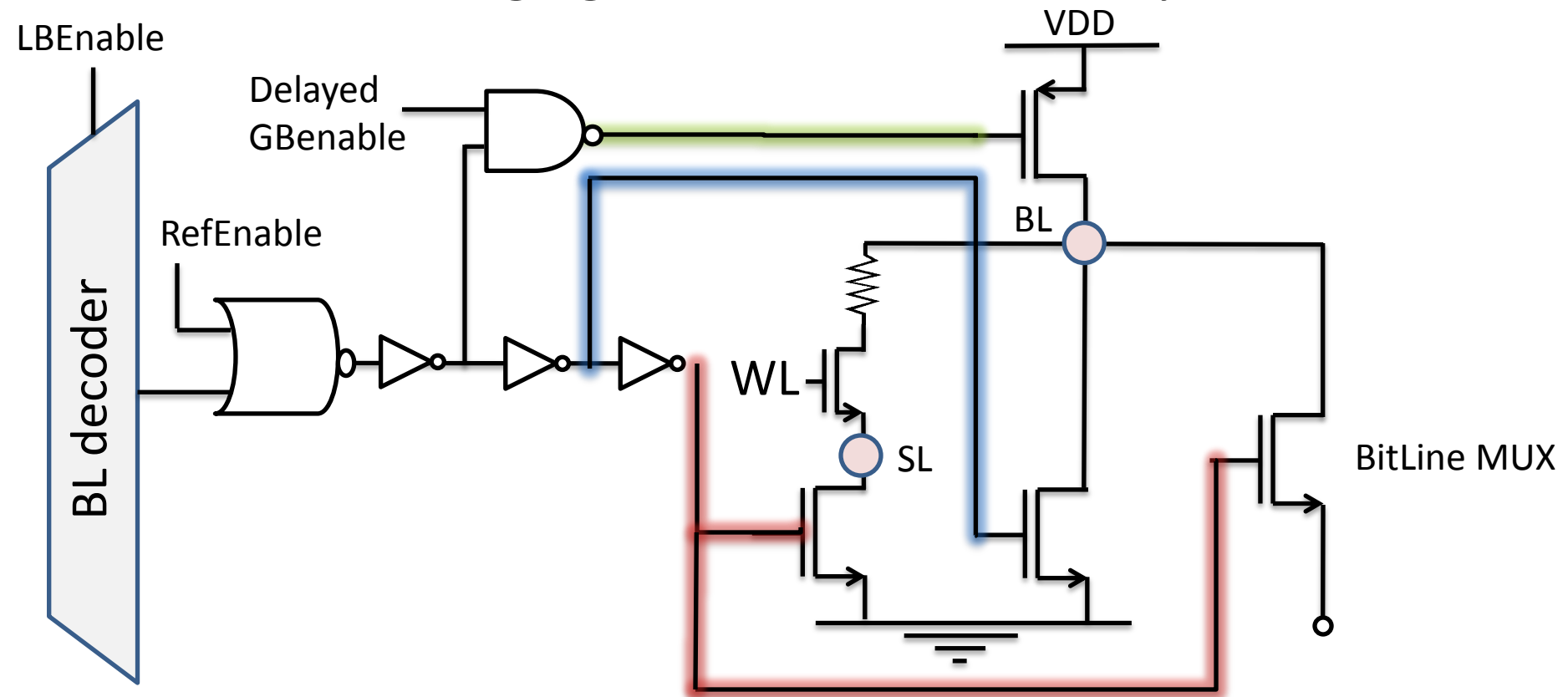- Invertors as delay elements
- Note: in case one Source Line Discharge per Local Block, Discharge gate connected to delayed LBEnable




Timing

 - RefEnable: AND-gated Gbenable + Lbenable
- Delayed Gbenable: inverter chain
- RefEnable connected to RefWL




Passgates

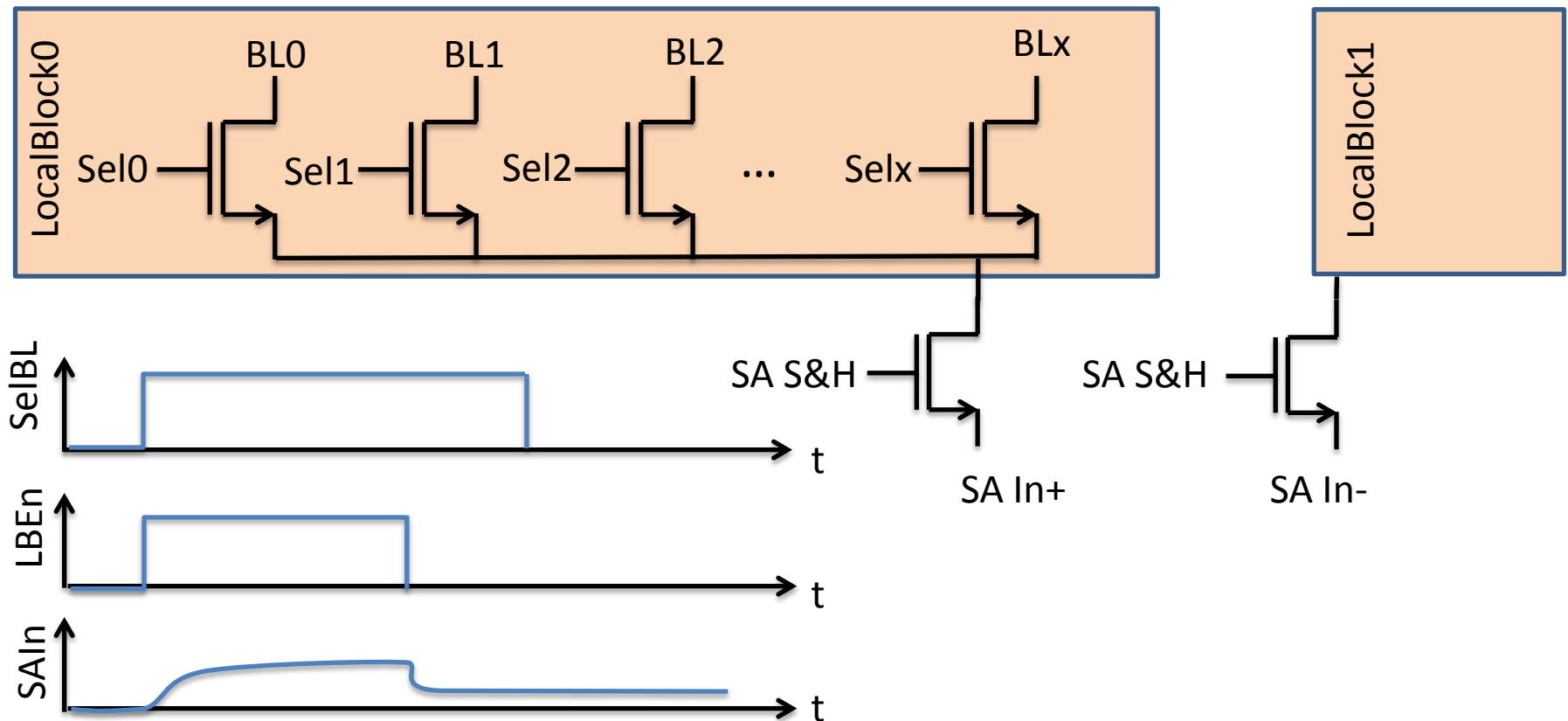- Just n-MOS (justified as long as $V_{\text{signal}} < 1V - V_t$)
- Low V_t !
- Timing so only one charge injection occurs



Line Drivers

 - AND-gates
- Passgates would leave nodes connected to digital circuits floated -> ill-advised



Future work

- Determine worst case decoder delay (MonteCarlo)
- Research optimal architecture parameters
Probably need to trim netlist to achieve acceptable simulation time
- Inverter chain to buffer RefEnable (huge load to drive)
- Optimize decoders? (and calculate decoder area)
- Automate timing signals for Sense Amplifier